
## **Application Note A60**
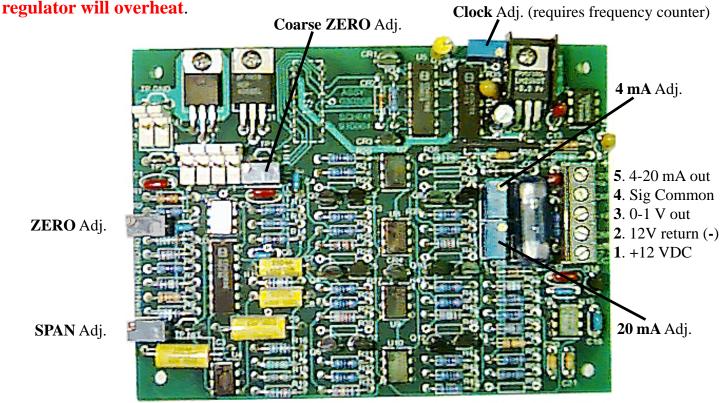
## **VALTRONICS** Model **2008 RT 12** volt & **24** volt powered versions

Shown below is a Model **2008 RT** type circuit board. It could be in a Model 2008LRTD-12VDC 1% CO<sub>2</sub> unit, a 2008HRTB-12VDC 5% CO<sub>2</sub> unit or a 2008HRTD-12VDC 20% CO<sub>2</sub> unit are examples of several differnt gas cell types and full scale ranges that are available. The difference between this **12VDC** powered version and a **24VDC** powered version consists of three (3) component changes: The 8 volt regulator chip (U11 a 7808 or LM340T8 type)in a **12VDC** powered sensor is replaced by a 12 volt regulator chip (7812 type or LM340T12 type). The jumper in location **R63** is replaced by a 5 ohm 3 watt resistor for a 24VDC powered version. Resistor **R8** changes from 7.5K (12V config) to 11.3K ohms. See page two for component locations.

Caution: A 12VDC configured unit will not operate properly on 24 VDC because the 8 volt



See the complete **specification sheet** for detailed operating specifications like a 2008**HRTB-24VDC 5%** CO<sub>2</sub> unit shown partially on page 2:

Gas: ..... Carbon dioxide (CO<sub>2</sub>)

Range: ...... 0-5% CO<sub>2</sub>

Accuracy: ......  $\pm 5\%$  of reading from mid to full scale ( $\pm 0.125\%$  CO, from 0-2..5% CO,)

Repeatability: ......  $\pm 1\%$  of full scale (challenge with same gas sample and assure zero )

Power Consumption: ...... 4 watts typical @ 24.0 VDC

Output Signals, voltage output: .. **0 to 1 volt** = 0 to 5% (linear scale data provided)


current loop output:... 4 to 20 mA = 0 to 5% ( linear scale data provided)500  $\Omega$  max loop resistance

3463 Double Springs Road • Valley Springs, CA 95252 • (209) 754-0707 • FAX (209) 754-0104


App Note A60, Model 2008 RT Troubleshooting • Page 1 of 3 • Revised: June 21, 1999
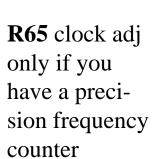
## Model 2008 RT 12V PC board

**R8** change from **7.5K** (12 v config) to **11.3K** for 24V



Model 2008 RT 24V PC board

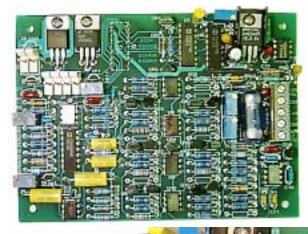




## 12 VDC Configuration

+8V regulator

✓ U11, 7808 or LM340T08

- R63 Jumper

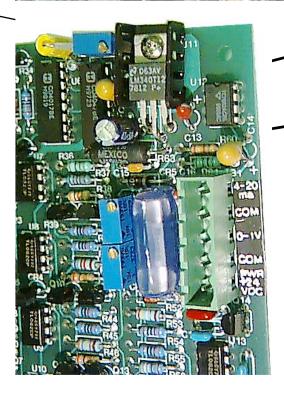

+12V regulator


U11, 7812 or LM340T12

-R63

5 ohm, 3 watt

24 VDC Configuration

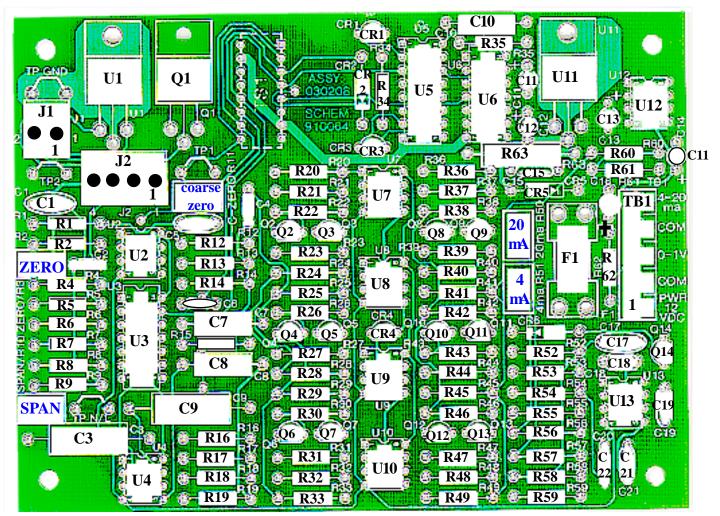The COARSE ZERO adjustment should only be done if you run out of adjustment range using the FINE ZERO adjustment (R3). Adjustments should be done very slowly since the output response is delayed about 8 to 10 seconds.



Reference **schematic** number **910070**. U11 is the main DC regulator (either 8V or 12V see page 2). U1 is the IR source 5Vregulator . Q1 switches the **IR source** ON and OFF. Continuity of the **IR source** may be measured using an ohmmeter across pins of J1 for about 3.5 ohms with power off. Clock U6 drives counter U5. The clock adjust R65 should only be done using a precision frequency counter for an **IR source** ON/OFF period of **1.4765** seconds. The **4 mA** adjustment (R51) should only be adjusted if the **ZERO** adjust (R3) is first adjusted with nitrogen in the gas cell for **0.000** volts out of the 0 to 1 volt output (pin #3 with respect to #4 of TB1). The **20 mA** adjustment (R50) should only be adjusted if the **SPAN** adjust (R10) is first adjusted with mid scale span gas in the gas cell for **0.500** volts out of the 0 to 1 volt output (pin #3 of TB1) then adjust 20 mA for an output of **12.0** mA. Use the scale data for you specific unit to look up the correct voltage and current loop outputs for the specific span gas level that you are using. As an example different than the mid-scale example given previously, if you have a Model 2008LRTB-12VDC **1.0%** CO<sub>2</sub> **full scale** unit and you have span calibration gas that is certified to 0.60 % CO<sub>2</sub> then you adjust SPAN for **0.600** volts out of the 0 to 1 volt output and then the **20 mA** adjustment for **13.60 mA** out of the 4-20 mA output (pin #5 with respect to #4 of TB1). The values of resistors R22, R26, R30, R37, R38, R42, and R46 are selected depending upon the full scale option.